

ALTERNATING CURRENT

classmate

Date _____
Page _____

$$V = V_0 \sin(\omega t + \phi)$$

(angular freq.) Initial phase

(Instantaneous voltage)

Phase
Voltage Amplitude
(Peak voltage)

$$P_{rms} = \frac{1}{(t_2 - t_1)} \int_{t_1}^{t_2} p(t) dt$$

(Any property) P

$$V_{rms}^2 = \frac{\int_t^{T+t} V^2 \sin^2(\omega t + \phi) dt}{(T+t) - t}$$

$$= \frac{V^2}{2T} \int_t^{T+t} (1 - \cos(2\omega t + 2\phi)) dt$$

$$= \frac{V^2}{2T} \left[t - \frac{\sin(2\omega t + 2\phi)}{2\omega} \right]_t^{T+t} = \frac{V^2}{2}$$


$$\Rightarrow V_{rms} = \frac{V}{\sqrt{2}}$$


V_{rms} is also called equivalent D.C Voltage

REMARK: Unless mentioned, volt. & current given for AC circuit are rms values.

NOTE

In Time period	$\rightarrow V_{rms}$
T	$V_0/\sqrt{2}$
T/2	$V_0/\sqrt{2}$
T/4	$V_0/\sqrt{2}$ only for \pm case

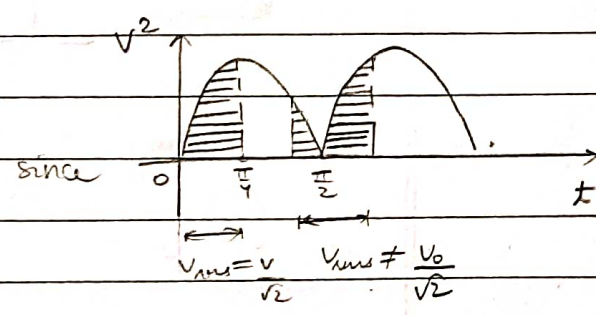

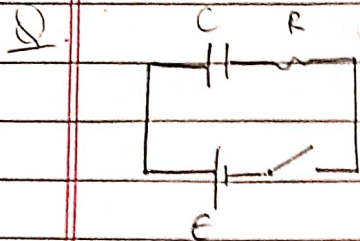

Switch closed at $t=0$.

Find i_{rms} for $t=0$ to RC

$$\underline{A} \quad E - \frac{q}{C} - iR = 0 \quad \Rightarrow \quad R \frac{dq}{dt} + \frac{q}{C} = E$$

$$\Rightarrow \quad q = EC (1 - e^{-\frac{t}{RC}})$$

$$\Rightarrow \quad i = \frac{E}{R} e^{-\frac{t}{RC}}$$

$$i_{rms}^2 = \left(\frac{\int_0^{RC} \frac{E}{R} e^{-\frac{t}{RC}} dt}{RC} \right)$$

$$V = V_0 \sin \omega t \quad \Rightarrow \quad P = Vi$$

$$i = i_0 \sin(\omega t + \phi)$$

$$P_{avg} = \int_0^T V_0 \sin \omega t \cdot i_0 \sin(\omega t + \phi) dt$$

$$= \frac{i_0 V_0}{2T} \int_0^T \cos \phi - \cos(2\omega t + \phi) dt$$

$$\Rightarrow \quad P_{avg} = \frac{i_0 V_0 \cos \phi}{2} = \left(\frac{i_0}{\sqrt{2}} \right) \left(\frac{V_0}{\sqrt{2}} \right) \cos \phi$$

$$= V_{rms} i_{rms} \cos \phi$$

(Power factor of AC circuit)


if $\cos \phi = 0 \Rightarrow P_{avg} = 0 \Rightarrow$ wattless current

Wattless component of current - $i \sin(\varphi)$
 (\because only $i \cos(\varphi)$ dissipates power)


→ Resistor

$$V - iR = 0$$
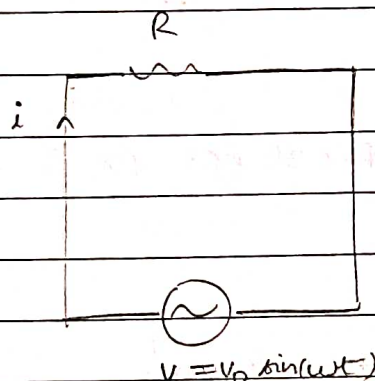
$$\Rightarrow i = \left(\frac{V_0}{R}\right) \sin \omega t$$




→ V & i in same phase!

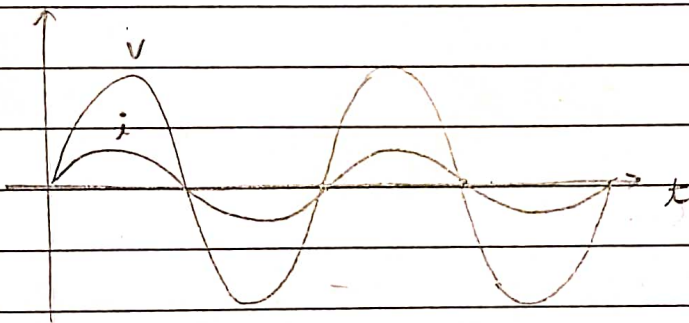

→ Capacitor


$$V - \frac{q}{C} = 0$$

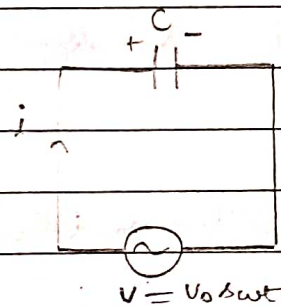

$$\Rightarrow q = V_0 C \sin \omega t$$

$$\Rightarrow i = \frac{dq}{dt} = V_0 C \omega \cos \omega t = \frac{V_0}{\left(\frac{1}{\omega C}\right)} \sin(\omega t + \frac{\pi}{2})$$

⇒ i leads v by $\pi/2$ ↑

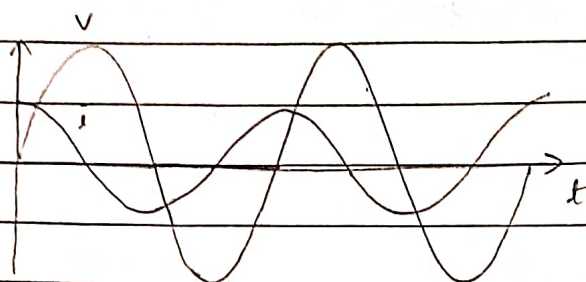

• Reactance (X_C) -


$X_C = \frac{1}{\omega C}$

→ Inductor

$$v - L \frac{di}{dt} = 0$$

$$\Rightarrow v = L i_0 \omega \cos \omega t$$
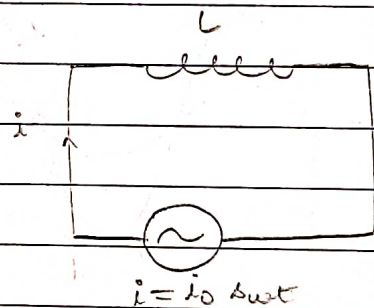
$$\Rightarrow v = i_0 (\omega L) \sin(\omega t + \frac{\pi}{2})$$



⇒ v leads i by $\pi/2$ ↑


• Reactance (X_L) -

$X_L = \omega L$

REMARK:

Reactance is a sort of resistance i.e. it does hinder current flow, yet circuit elements with reactance do not consume power.

L-C-R SERIES CIRCUIT

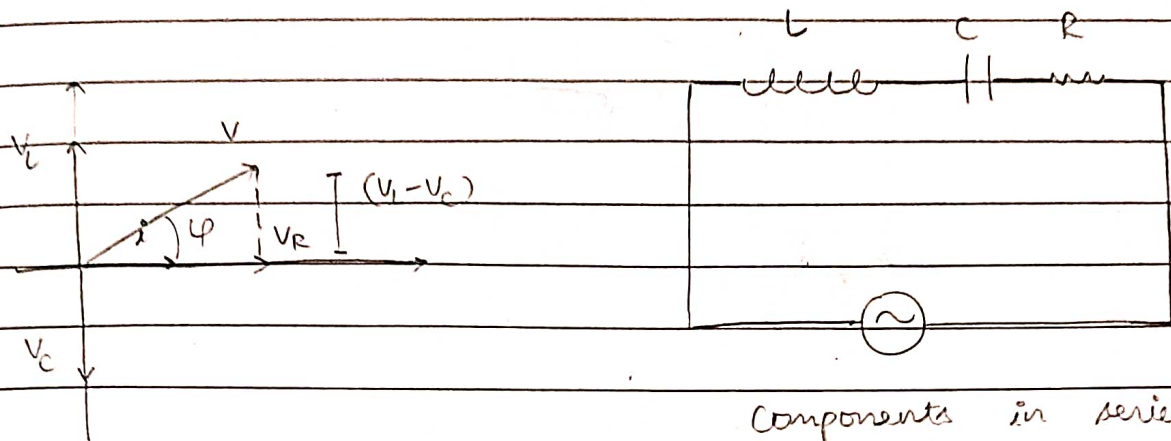

Components in series

↓
Current in phase

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$Z = \frac{V}{i} = \sqrt{\left(\frac{V_R}{i}\right)^2 + \left(\frac{V_L - V_C}{i}\right)^2} \Rightarrow Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan(\phi) = \frac{V_L - V_C}{V_R} = \frac{(X_L - X_C)}{R} \Rightarrow \cos\phi = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{R}{Z}$$

$$P = V_{rms} \cdot i_{rms} \cos\phi = V_{rms} \cdot i_{rms} \cdot \frac{R}{Z}$$

$$= i_{rms}^2 R$$


→ Series Resonance

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$Z_{min} = R \quad \text{at} \quad \omega = \frac{1}{\sqrt{LC}}$$

This ω is called resonant/natural freq

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

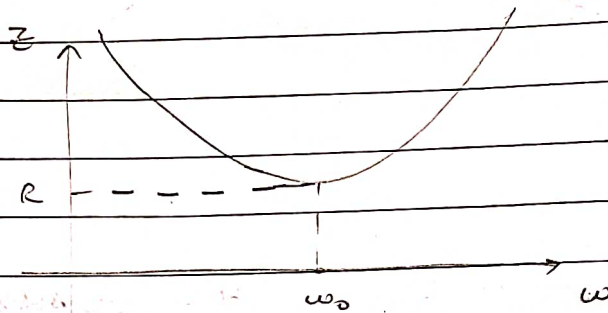

$\Delta \omega < \omega_0$, $X_C > X_L \Rightarrow i$ leads V

$\Delta \omega > \omega_0$, $X_L > X_C \Rightarrow V$ leads i


if $V = V_0 \sin \omega t$ & $\tan \phi = \frac{X_L - X_C}{R}$

$$\Rightarrow i = \left(\frac{V_0}{Z} \right) \sin(\omega t - \phi)$$

$\because X_L > X_C \Rightarrow V$ leads i
by ϕ

In resonance,

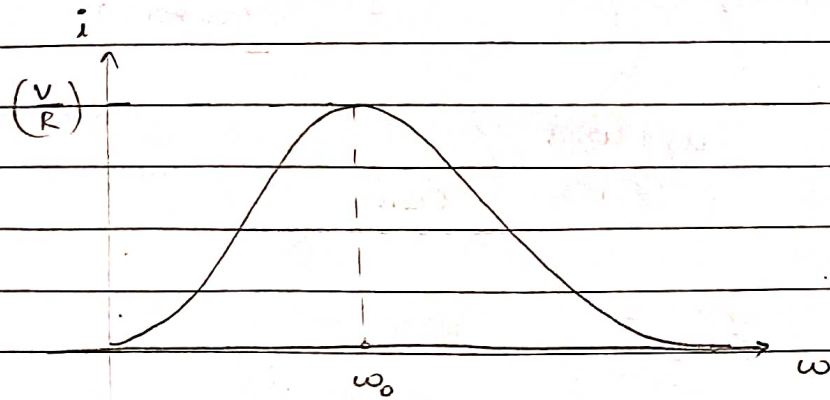- i & V in same phase i.e. $\tan \phi = 0$
- $Z = Z_{\min}$
- $P = P_{\max}$
- $i = i_{\max}$




- Sharpness of resonance - How easily resonance freq is distinguishable from neighbouring freq.

- Quality factor (Q-factor) -

$$Q = \frac{\omega_0}{\Delta\omega}$$

(Bandwidth)

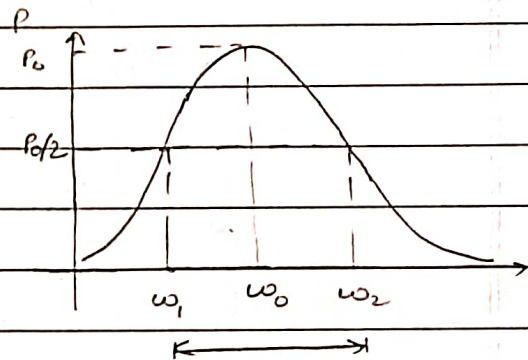

at $\omega = \omega_1$ & ω_2

$$P = P_0/2$$

$$\& i = i_0/\sqrt{2}$$

Bandwidth of resonance $\Delta\omega = (\omega_2 - \omega_1)$

$$\sqrt{2}R = \sqrt{R^2 + \left(\frac{1}{\omega_1 C} - \omega_1 L\right)^2}$$

$$\Rightarrow \frac{1}{\omega_1 C} - \omega_1 L = R \quad \text{--- (i)} \quad (\omega_1 < \omega_0 \Rightarrow \omega_C > \omega_L)$$

$$\text{Similarly, } \omega_2 L - \frac{1}{\omega_2 C} = R \quad \text{--- (ii)} \quad (\omega_2 > \omega_0 \Rightarrow \omega_C < \omega_L)$$

$$(i) - (ii) \Rightarrow \frac{1}{C} \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) = L(\omega_1 + \omega_2)$$

$$\Rightarrow (\omega_1 + \omega_2) \left(\frac{1}{C\omega_1\omega_2} - L \right) = 0$$

$$\omega_1 + \omega_2 \neq 0 \Rightarrow \omega_1\omega_2 = \frac{1}{LC}$$



$$(i) + (ii) \Rightarrow \frac{1}{C} \left(\frac{1}{\omega_1} - \frac{1}{\omega_2} \right) + L(\omega_2 - \omega_1) = 2R$$

$$\Rightarrow \omega_2 - \omega_1 = \left(\frac{R}{L} \right)$$

$$\Rightarrow Q = \frac{\omega_0 L}{R} = \frac{\omega_0 C}{R} \quad (\text{reactance at resonance})$$

PARALLEL L-C-R CIRCUIT

Here, voltage in same phase

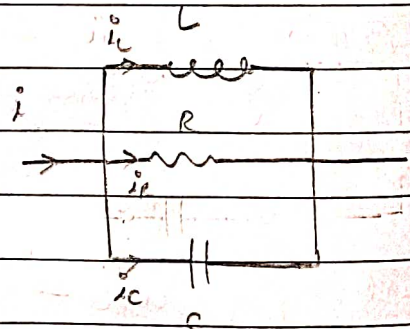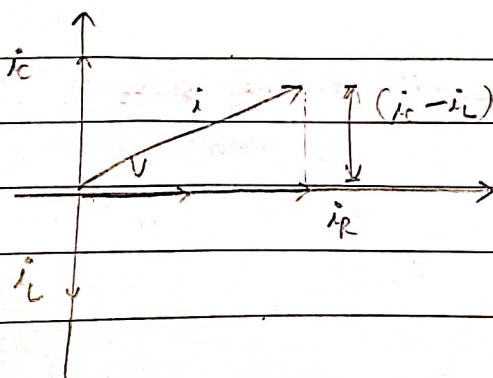


$$i = \sqrt{i_R^2 + (i_C - i_L)^2}$$

$$\Rightarrow \frac{V}{Z} = \sqrt{\left(\frac{V}{R}\right)^2 + \left(\frac{V}{X_C} - \frac{V}{X_L}\right)^2} \Rightarrow$$


$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}$$

Q

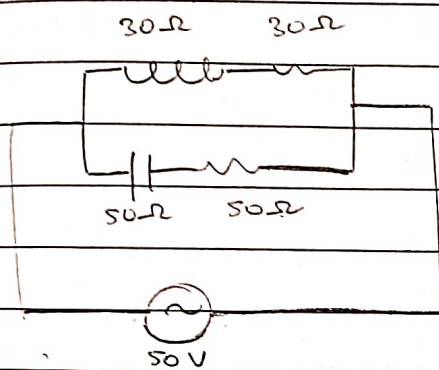

find current
in circuit &
impedance of circuit

A.

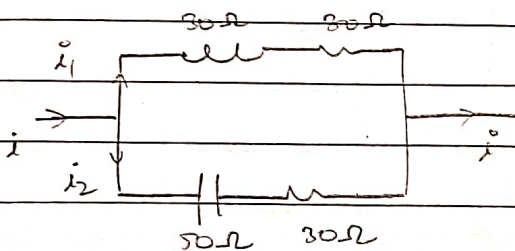


$$Z_{LR} = \sqrt{R^2 + X_L^2} = 30\sqrt{2}$$

$$Z_{RC} = \sqrt{R^2 + X_C^2} = 50\sqrt{2}$$


$$i_{LR} = \frac{V}{Z_{LR}} = \frac{5}{3\sqrt{2}}$$
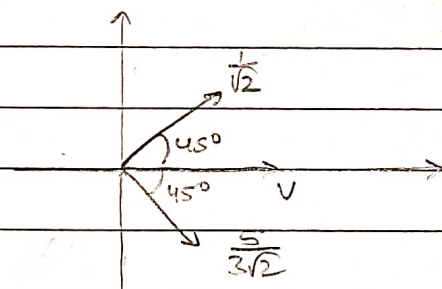
$$i_{RC} = \frac{V}{Z_{RC}} = \frac{1}{\sqrt{2}}$$



$$k_{\phi LR} = \frac{X_L}{R} = \frac{30}{30} = 1$$

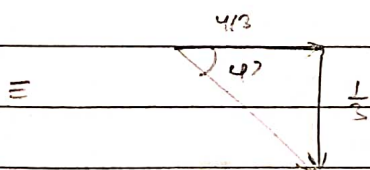$\Rightarrow \phi_{LR} = \frac{\pi}{4} \Rightarrow i_1$ lags
V by $\pi/4$



$$k_{\phi RC} = \frac{X_C}{R} = \frac{50}{30} = 1$$

$\Rightarrow \phi_{RC} = \frac{\pi}{4} \Rightarrow i_2$ leads
V by $\pi/4$

$$i = \frac{\sqrt{17}}{3}$$


$$Z = \frac{V}{i} = \frac{150}{\sqrt{17}}$$

→ Complex impedance method

$R \rightarrow R$

$X_L \rightarrow j\omega L$

$X_C \rightarrow -j/\omega C$

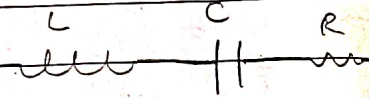


where $j = \sqrt{-1}$

Now, treat all components as resistors.

So, $Z = R + j\omega L - \frac{j}{\omega C}$
 (complex impedance)


(Impedance of circuit) = $|Z|$

Q.

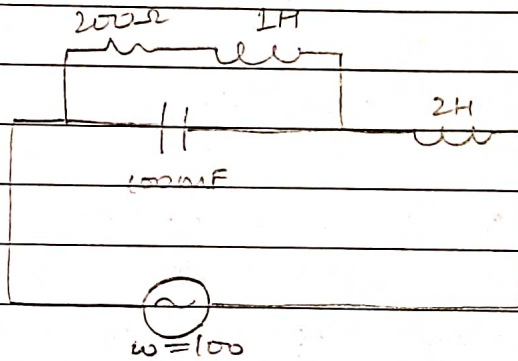

Find impedance.

A.

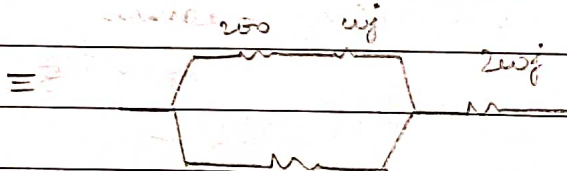

$Z = \frac{1}{\left(\frac{1}{200 + 100j}\right) + (10j)} + 200$


NOTE:

$$\frac{1}{Z} = \frac{1}{X_C} - \frac{1}{X_L}$$

In resonance, $Z = \infty$

So, no current flows through circuit.

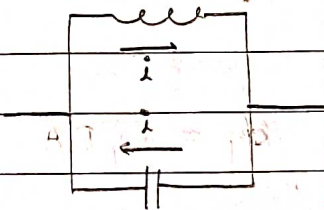Hence, this combination behaves as an open switch.



→ Net current flow = 0

AC INSTRUMENTS


→ Hot wire (voltmeter & Ammeter)

- Based on heating effect of current

- Graduations of scale are not uniform since i^2 or V^2 is being measured instead of i or V

→ Transformer


Circuit diagram

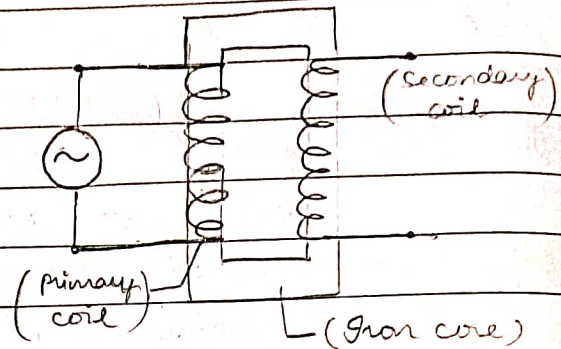 $V_{out} < 1 \Rightarrow$ step-down V_{in} $V_{out} > 1 \Rightarrow$ step-up V_{in} 

$$\Phi_p = N_p BA \quad \Rightarrow \quad V_i = \frac{d\Phi_p}{dt} = N_p A \frac{dB}{dt}$$

$$\Phi_s = N_s BA \quad \Rightarrow \quad V_o = -\frac{d\Phi_s}{dt} = -N_s A \frac{dB}{dt}$$

$$V_o = -\left(\frac{N_s}{N_p}\right) V_i$$


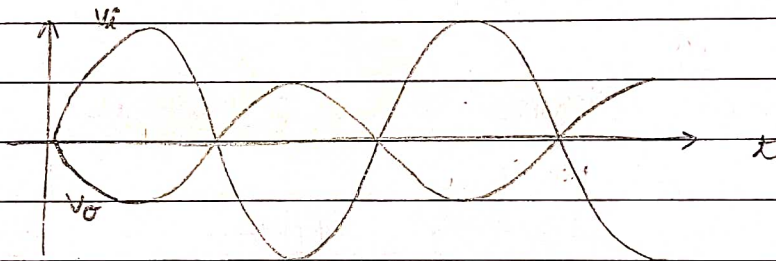
Ideally, $P_{in} = P_{out}$

But a fraction of power is lost due to :-

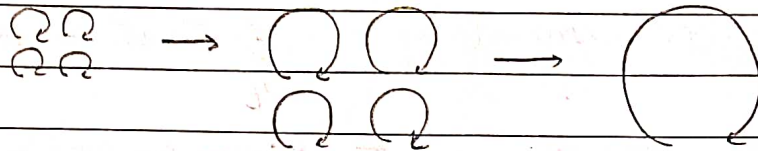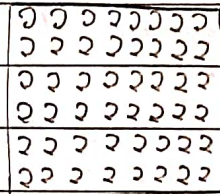- 1) Joule heating
- 2) Magnetic hysteresis loss
- 3) Eddy currents

- Eddy currents - Small loops of current form in the core as flux through it changes


Eddy currents in boundaries of neighbouring loops combine to form larger loops of current



→ AC & DC Generator


$$\phi = NBA \cos \omega t$$
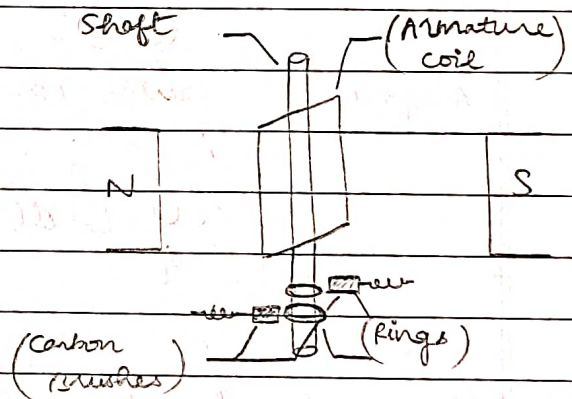
$$V = -\frac{d\phi}{dt} = NBA \omega \sin \omega t$$



AC generator

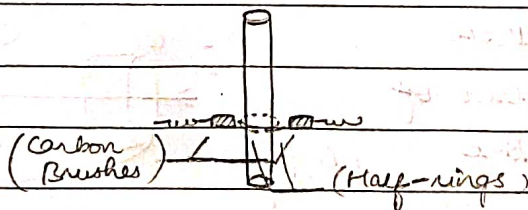To convert this to DC generator, we replace 2 full rings with 2 half-rings. This set-up gives uni-directional current



EM WAVES

→ Maxwell's Eqⁿs

1) Gauss law : $\oint_S \vec{E} \cdot d\vec{S} = \frac{q_{\text{enclosed}}}{\epsilon_0}$

2) $\oint_S \vec{B} \cdot d\vec{S} = 0$

3) Ampere's Circuital law : $\oint_L \vec{B} \cdot d\vec{l} = \mu_0 i_{\text{threaded}}$

4) Faraday's law : $\oint \vec{E} \cdot d\vec{l} = -\left(\frac{d\phi}{dt}\right)$

→ Inconsistency in Ampere's law


Ampere's law can be written as

$$\oint_L \vec{B} \cdot d\vec{l} = \mu_0 \int_S \vec{J} \cdot d\vec{A}$$

where the surface S over which the flux of \vec{J} is evaluated can be any open surface bounded by the Amperian loop L .

Consider a || plate cap. being charged

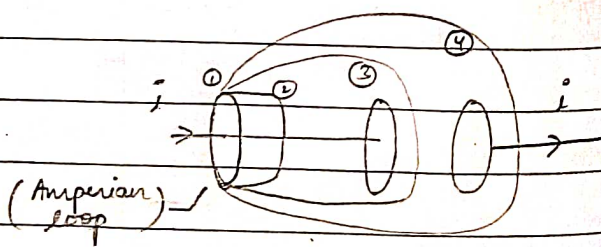For each of these surfaces, the flux of \vec{J} should give the same current



As evident, surfaces 1, 2, 4 are pierced by the current i .

However, no current passes through 3.

To remove this inconsistency, we propose the existence of a displacement current 'flowing' b/w the plates of the cap.

This disp. current should be equal to the conduction current (i) entering the surface 3.

$$\oint_S \vec{J} \cdot d\vec{A} = i = \frac{dq}{dt} = \frac{d}{dt} \left(\epsilon_0 \oint_S \vec{E} \cdot d\vec{A} \right)$$

$$= \epsilon_0 \frac{d\phi_E}{dt}$$

\therefore If we define $i_d = \epsilon_0 \frac{d\phi_E}{dt}$

$$\times \quad i_{\text{total}} = i + i_d$$

Ampere's law becomes

$$\oint_L \vec{B} \cdot d\vec{l} = \mu_0 i_0 + \mu_0 \epsilon_0 \frac{d\phi_E}{dt}$$

As a consequence of this modification, changing \vec{E} can produce \vec{B}

Changing \vec{B} produces \vec{E}
 Changing \vec{E} produces \vec{B}

If \vec{E}/\vec{B} is produced in space,
 the disturbance is carried forward.

This is known as EM wave.

- Wavefront — A surface where all waves are in same phase at a particular time.

Dirⁿ of propagation of wave is normal to wavefront.

$$\left. \begin{aligned} \vec{E} &= E_0 \sin(\omega t - kx) \hat{e}_1 \\ \vec{B} &= B_0 \sin(\omega t - kx) \hat{e}_2 \end{aligned} \right\} \text{ in phase, where } \hat{e}_1 \cdot \hat{e}_2 = 0$$

\vec{E} , \vec{B} , \vec{c} are mutually \perp

└ (dirⁿ of propagation of EM wave)

$$\text{So, } \hat{c} = \hat{E} \times \hat{B}$$

E_0 & B_0 are related by

$$\frac{E_0}{B_0} = c$$

where

$$c = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$$

in vacuum

For a medium,

$$c = \frac{1}{\sqrt{\mu_0 \mu_r \epsilon_0 \epsilon_r}}$$

$$\Rightarrow c' = c = \frac{c}{\sqrt{\mu_r \epsilon_r}}$$

(Refractive index)

relative Permittivity
relative Permeability

• Avg. Energy density - $\int \left(\frac{\epsilon_0 E^2}{2} + \frac{B^2}{2\mu_0} \right) dV$


$$= \int dV$$

$$\Rightarrow \left(\frac{1}{2} \right) \left(\frac{\epsilon_0 E_0^2}{2} + \frac{B_0^2}{2\mu_0} \right) = \frac{1}{2} \epsilon_0 E_0^2$$

$$= \frac{B_0^2}{2\mu_0}$$

Power transferred
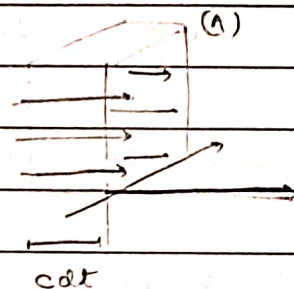
$$= (Acdt) \left(\frac{1}{2} \epsilon_0 E_0^2 \right)$$



• Intensity - Power transferred per unit normal area

$$\Rightarrow I = \frac{1}{2} \epsilon_0 E_0^2$$

$$= \frac{1}{2} \frac{E_0 B_0}{\mu_0}$$

• Poynting vector -

$$\vec{S} = \frac{\vec{E} \times \vec{B}}{\mu_0}$$

$$= \vec{E} \times \vec{H}$$

Poynting vector contains info. about instantaneous power transmitted & dirⁿ of propagation of wave.


• Force exerted by EM wave -

$$\left(\begin{array}{l} \text{Momentum} \\ \text{of} \\ \text{wave} \end{array} \right) \left\{ \begin{array}{l} p = \frac{E}{c} \leftarrow \text{Energy} \\ \quad \quad \quad \leftarrow \text{speed of light} \end{array} \right.$$

Let us consider an area absorbing light

$$P_i = \left(\frac{IAc_0}{c} \right) dt$$

$$P_f = 0$$

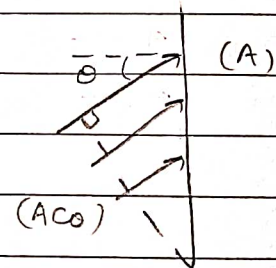


$$\Rightarrow \frac{dp}{dt} = \left(\frac{IA}{c} \right) c_0 \Rightarrow F_{\text{abs}} = \left(\frac{IA}{c} \right) c_0$$

{ This force is directed along dirⁿ of wave. }

If the area was reflecting light instead;

$$dp = 2pc \cos \theta dt = 2 \left(\frac{IA \cos \theta}{c} \right) c \theta dt$$
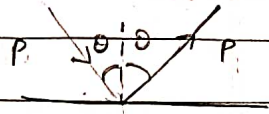
$$\Rightarrow \frac{dp}{dt} = \frac{2IAC \cos^2 \theta}{c}$$



$$\Rightarrow \left. \begin{array}{l} F_{\text{ref}} = \frac{2IAC \cos^2 \theta}{c} \end{array} \right\} \begin{array}{l} \text{This force is directed} \\ \text{along normal to surface} \end{array}$$

• Radiation/Radiant Pressure -

$$P_{\text{abs}} = \frac{F_{\text{abs}}}{A} = \left(\frac{I c \cos^2 \theta}{c} \right)$$

$$\therefore P = \frac{F_{\perp}}{A}$$

$$P_{\text{ref}} = \frac{F_{\text{ref}}}{A} = \left(\frac{2I c \cos^2 \theta}{c} \right)$$